

Lab session Adders

Group A: October 12, 2009

Group B: October 13, 2009

Work in the given groups of two. Submit your solutions to the respective assignment on Blackboard. The file name is:

`a02_sXXXXXX_sXXXXXX.tar.gz`

One of the group members commits your solution. The other(s) submit a txt-file with a confirmation. Keep an eye on the deadline (see Blackboard)!

1 Project

Read section C.6 of Appendix C.

1. Build a 1-bit full adder (with carry in and carry out).
 - (a) Determine the inputs and outputs of a 1-bit full adder and build a truth table.
 - (b) Convert the truth table to Boolean algebra, and optimize the Boolean expression.
 - (c) Implement the Boolean expression as a circuit called "1-Bit Adder" in Logisim.
2. Build a circuit of an 8-bit adder.
 - (a) Use 1-bit adders to create an 8 bit adder, that adds two 8-bit wide inputs.
3. Build a circuit of an 8-bit two's complement adder.
 - (a) Think about a way how overflow can be determined from carry outs. Overflow happens for example in these cases: $127 + 1 = -128$ or $-128 + (-1) = 127$.
 - (b) Build a circuit of an 8-bit two's complement adder that has an extra output bit, denoting overflow.
4. Build a circuit of an 8-bit two's complement carry lookahead adder using 4 2-bit adder blocks.

- (a) What are the "super propagates" and the "super generates", and C1, C2, C3 and C4 values for the addition of numbers 11001011 and 01111100 (see Appendix C page C-44). Calculate the carry out of the most significant bit (i.e. c_8).
- (b) Build a circuit for a 2-bit adder block. This block has input carryIn, a_0 , a_1 , b_0 and b_1 , and outputs s_0 , s_1 , P_0 , G_0 . Note that there is no output for carryOut, as a carry lookahead adder doesn't use c_{i-1} .
- (c) Build a circuit of the 8-bit two's complement carry lookahead adder by creating a "carry lookahead unit" that uses 4 of your own 2-bit adder blocks.
- (d) On this 8-bit adder circuit, create an extra output bit, denoting overflow. You will have to create a variant of your last 2-bit adder block.
- (e) To compare the carry lookahead 8-bit adder and the ripple carry 8-bit adders, count the maximum number of gate delays, i.e. the maximum number of AND and OR gates a signal passes in both adders.