

Computer Systems and -architecture

Project 5

1 Ba INF 2013-2014

Bart Meyers
bart.meyers@ua.ac.be

Don't hesitate to contact the teaching assistant of this course. You can reach him in room M.G.3.17 or by e-mail.

Time Schedule

Projects are solved in pairs of two students. Projects build on each other, to converge into a unified whole at the end of the semester. During the semester, you will be evaluated three times. At these evaluation moments, you will present your solution of the past projects by giving a demo and answering some questions. You will immediately receive feedback, which you can use to improve your solution for the following evaluations.

For every project, you submit a small report of the project you made by filling in `verslag.html` completely. A report typically consists of 500 words and a number of drawings/screenshots. Put all your files in a tgz archive, as explained on the course's website, and submit your report to the exercises on Blackboard.

- Report deadline: **December, 1 2013, 23u55**
- Evaluation and feedback: **December, 3 2013**

Project

Read sections 4.1, 4.2, 4.3 and 4.4 of Chapter 4. You can use all Logisim libraries for this assignment.

1. Build a circuit that implements a **16-bit program counter (PC)** that selects an instruction in a RAM element of 16-bit words. Use the Logisim `SD_GroupXX.circ` file provided on the course page. Rename the file so that 'XX' is your group number. Use your 16-bit register. By default, the PC is increased each clock cycle, and the next instruction is read from memory. In case of a relative branch, the PC is increased, and then the branch value is added as a 2's complement value (e.g., if the PC has value 10 and the next cycle there is a branch of value 5, then the next PC value is 16, not 15). In case of an absolute branch (or jump) the PC is directly set to the branch value. You should have the following inputs and outputs:

name	in/out	width	meaning
branch relative?	I	1 bits	branch to relative value?
branch absolute?	I	1 bits	branch to absolute value? (cannot be 1 if branch relative? is 1)
branch value	I	16 bits	the value that is used in case of a branch
C	I	1 bit	clock input
reset	I	1 bit	if set, the PC is reset to 0
instruction address	O	16 bits	the address of the instruction in the instruction memory

2. Use your register file, a *data* RAM element (16-bit addresses, 16-bit words), your program counter with *instruction* RAM element (16-bit addresses, 16-bit words), and your own ALU to implement a partial datapath. *Copy* the program counter in your circuit instead of using it as a block. Implement your datapath in the “main” circuit in `SD_GroupXX.circ`. You will have to modify your register file first so that it has an output for every register, to connect to the outputs in the “main” circuit.

- The datapath must be able to perform so-called register operations. These are the 9 operations you implemented in your ALU. This time, operands are read from, and the result is stored into registers. The right registers are selected by specifying the *rs*, *rt* and *rd* index inputs in your register file. For binary operations (i.e., *and*, *or*, *add*, *lt*, *gt*, *eq*), the registers are used as follows:

$\$rd = \$rs \text{ operation } \$rt$

For unary operations (i.e., *inv*, *not*), the registers are used as follows ($\$rt$ is unused):

$\$rd = \text{operation } \rs

For the zero instruction, the registers are used as follows:

$\$rd = 0$

The 16-bit instructions for the register operations are formatted as follows:

- 15-12 : operation code
- 11-8 : $\$rd$
- 7-4 : $\$rs$
- 3-0 : $\$rt$

Example: To add the values of register 1 and register 2, and put the result in register 10, the following instruction is loaded:

15	14	13	12	11	10	9	8	7	6	5	4	3	2	1	0
0	1	0	0	1	0	1	0	0	0	0	1	0	0	1	0

- The datapath must be able to perform the load word (*lw* – reading from *data* RAM, op-code 1110) and store word (*sw* – writing to *data* RAM, op-code 1111) operations. These are immediate instructions, and similar to the MIPS *lw/sw* instructions, a constant can be used to denote an offset (the offset is unsigned, as opposed to the MIPS *lw/sw* instructions). The meaning of these instructions is as follows:

lw: $\$rt = \text{MEM}[\$rs + \text{offset}]$

sw: $\text{MEM}[\$rs + \text{offset}] = \rt

The 16-bit instructions for the memory operations are formatted as follows:

- 15-12 : *lw/sw* operation op code (resp., 1110 or 1111)
- 11-8 : $\$rs$
- 7-4 : $\$rt$
- 3-0 : memory index offset for the *lw/sw* operations

Example: To store the value of register 3 in memory, 4 address spaces beyond the address stored in register 2:

15	14	13	12	11	10	9	8	7	6	5	4	3	2	1	0
1	1	1	1	0	0	1	0	0	0	1	1	0	1	0	0

- You can try out your datapath by editing your RAM-elements. You can do this by right-clicking them and selecting edit contents or save/load image.

3. Create and run a test file for your simple datapath. You will do this by creating a file with tests, and running it on your circuit using the program `Test.py`. You need to install Python (<http://python.org/download/releases/2.7.3/>) to run `Test.py`. Download `Test.py`, `SDTest_GroupXX.txt` (from the course page) and `logisim-generic-2.7.1.jar` (<http://sourceforge.net/projects/circuit/files/2.7.x/2.7.1/>) and save in the same folder as your adapted `SD_GroupXX.circ` project (you already have created `SD_GroupXX.circ` in the previous assignment). The program takes a file containing small assembler programs that are datapath tests as input, and a `SD_GroupXX.circ` logisim file. It runs all datapath tests and reports test failures. For this assignment you will have to do the following:

- Create your datapath test file by adding lines to `SDTest_GroupXX.txt`. It already contains a simple test:

```
LOADMEM
lw r0 r1 4 # loads a[0] into r1
lw r0 r2 5 # loads a[1] into r2
add r3 r1 r2 # put a[0]+a[1] into r3
DATAMEM
1024
-1
CHECKMEM
r3: 1023
pc: 3
END
```

The test involves three instructions: two times loading and an addition (below `LOADMEM`). When running the test, the `LOADMEM` part is assembled into binary strings (in this case three strings). Then, the `DATAMEM` adds a 0-instruction that will cause the simulator to halt here. Subsequently, a data part is provided with two numbers (below `DATAMEM`). In total, we have now six binary strings: the three first are instructions, then a `STOP`-instruction, then two data strings. These are loaded into *both* your instruction RAM and your data RAM. So you will have to write your tests as if your architecture was a stored-program architecture: where the program and the data are in the same memory element. So you will have to be aware that you can reference and alter your program instructions!

In this case, the word in memory address 4 (which is 1024) will be loaded into r1, and the word in memory address 5 (which is -1) will be loaded into r2. Then, r1 and r2 are added, and the result is stored in r3, so r3 should contain the value 1023. The actual tests are written below `CHECKMEM`: here we check whether r1 contains the value 1023 and whether the program counter has value 3. You can check the value of the pc and any registers (unfortunately not of memory contents - you will have to load them into a register to check them). The check is performed after the last instruction (in this case, the addition). The test is ended by the `END`-line.

You can add multiple test programs to the same file, by simply starting a new `LOADMEM` after the `END`. You can also perform checks at a specific point in your code, by adding a `DATAMEM` block at that point. To test the `lw`-instruction more thoroughly we can alter the above test as follows:

```
LOADMEM
lw r0 r1 4 # loads a[0] into r1
CHECKMEM
r1: 1024
LOADMEM
```

```

lw r0 r2 5 # loads a[1] into r2
CHECKMEM
r2: -1
LOADMEM
add r3 r1 r2 # put a[0]+a[1] into r3
DATAMEM
1024
-1
CHECKMEM
r3: 1023
pc: 3
END

```

Your goal is to add significant tests to `Test.GroupXX.txt`. Write *a lot* of tests. The following are the operations you should implement in your simple datapath and thus test in your test file:

- zero \$rd: \$rd = 0
- and \$rd, \$rs, \$rt: \$rd = \$rs AND \$rt
- or \$rd, \$rs, \$rt: \$rd = \$rs OR \$rt
- not \$rd \$rs: \$rd = ! \$rs
- add \$rd, \$rs, \$rt: \$rd = \$rs + \$rt
- inv \$rd \$rs: \$rd = - \$rs
- lt \$rd, \$rs, \$rt: \$rd = \$rs < \$rt
- gt \$rd, \$rs, \$rt: \$rd = \$rs > \$rt
- eq \$rd, \$rs, \$rt: \$rd = \$rs == \$rt
- lw \$rs, \$rt, c: \$rt = MEM[\$rs + c]
- sw \$rs, \$rt, c: MEM[\$rs + c] = \$rt

- All files must be in the same directory. The program must be executed from the console as follows:

```
python Test.py -s SDTest.GroupXX.txt SD.GroupXX.circ
```

with `SDTest.GroupXX.txt` as the file containing your datapath tests and `SD.GroupXX.circ` as your logisim file (change XX to your group number). Some lines will be outputted to the console, ending with a line denoting how many tests were executed (depending on how many test lines you have added to your file) and how many of them failed or produced an error (you should have 0 here).

If not successful, tests can be 'errors' or 'failures'. An error means that some of the resulting signals were 'Error' signals or 'don't care' signals ('E' or 'x', or a red/blue signal line in logisim). A failure means that the expected result did not match what you have specified in your test. If you have failure or error tests, there will be some information about this failure/error in the output.

- If your tests fail while you expect them to be successful, try the following:
 - (a) Double-check your solution to make sure that there is no error in your datapath. Make sure that you have connected your register file to the register outputs correctly!
 - (b) The script has generated some file(s) named `SDTest.GroupXX.textX`, which contain the compiled hexadecimal version of each test program you wrote in `SDTest.GroupXX.txt`. In Logisim, use these generated `SDTest.GroupXX.textX` files to load them in

your RAM-element (right-click your RAM-element, select “load image”). Check whether the outcome is correct. If this is the case but the corresponding test failed when executed with the script, it means that there is something wrong with the execution of the script, so continue with step c.

- (c) Check the corresponding `SDTest_GroupXX.reportX` file. The file is a printout of the simulation in Logisim of the corresponding test. It can be read line per line as follows: the first 16 bits is the pc value at a given clock tick, the remaining sixteen 16 bits are the register values (r0 to r15) at this clock tick. Since your pc should increase every clock tick, the first column should also increase by one on each line. If this is not the case, and some pc values appear twice below each other, this probably means that values are only read at the rising edge. In this case, please check your registers (i.e., D-Flipflops used in your register) in Logisim and make sure they are all edge-triggered on the falling edge.
- (d) If you still have not found the error, you might have hit a bug in the Logisim simulator that only occurs on some platforms. This bug can be resolved as follows: try starting every test program with `zero r1` (don’t forget to also update address values as the whole program shifts by one...). For some reason, the Logisim simulator does not seem to be able to handle certain calculations on the first clock tick on some platforms.
- (e) If you experience “random” bugs where in some test runs your test fails, but in others your test passes, then the following should resolve this: in Logisim, disable the option Project→Options→simulation tab→Add Noise to component delays.