

Computer Systems and -architecture

Project Exam Retake

1 Ba INF 2020-2021

Brent van Bladel
brent.vanbladel@uantwerpen.be

Don't hesitate to contact the teaching assistant of this course. You can reach him in room M.G.305 or by e-mail.

Time Schedule

Projects are solved individually. Projects build on each other, to converge into a unified whole at the end of the semester. At the evaluation moment, you will present your solution by giving a demo and answering some questions.

You will submit a solution for all seven projects from the first semester, with the differences explained in this project description. Covering all seven projects, you submit one report by filling in `verslag.html` completely. A report typically consists of 1000 words and a number of drawings/screenshots. Put all your files in one `tgz` archive, as explained on the course's website, and submit your report to the exercises on Blackboard.

Project

Extend your datapath to support data words (in register and data memory) of 20 bit. Aside from changes to the datapath itself, this will require changes to:

- ripple-carry adder and carry-lookahead adder
- ALU (and all ALU instructions)
- register and register file

The instruction set your datapath supports remains the same. Note that the `ori` operation still only operate on the lower 8 bits, and the `lui` operation still only operates on the upper 8 bits.

Make sure you use `TestRetake.py` for this project. As always, if you have questions about the script, cannot get it to work or suspect that there is a bug, contact the teaching assistant.