Computer Systems and -architecture

Retake project

1 Ba INF 2022-2023

Kasper Engelen kasper.engelen@uantwerpen.be

Time Schedule

Projects are solved individually. At the evaluation moment, you will present your solution by giving a demo and answering some questions. The date and location of the evaluation moment will be communicated later on.

You will submit a solution for all seven projects from the first semester, with the differences explained in this project description. Covering all seven projects, you submit one report by filling in verslag.html completely. A report typically consists of 1000 words and a number of drawings/screenshots. Put all your files in one tgz or zip archive, as explained on the course's website, and submit your report to the exercises on Blackboard. The assignment has to be handed in on Wednesday 16 August 2023, 22h00.

Project

Extend your datapath to support data words (in register and data memory) of 20 bit. Aside from changes to the datapath itself, this will require changes to:

- ripple-carry adder and carry-lookahead adder
- ALU (and all ALU instructions)
- register and register file

The instruction set of your datapath remains the same. Note that the ori operation still only operates on the lower 8 bits, and the lui operation still only operates on the upper 8 bits. The other assignments remain the same.

Example: if we do "lui r1 1" then r1 will be equal to 4096. In binary this is equal to:

 $0000 \ 0001 \ 0000 \ 0000 \ 0000$

Make sure you use TestRetake.py for this project. You will have to write new tests that are suited to 20-bit arithmetic. Also make sure you use the 20-bit versions of ALU_GroupXX and SD_GroupXX. As always, if you have questions about the script, cannot get it to work, or suspect that there is a bug, please contact the teaching assistant.