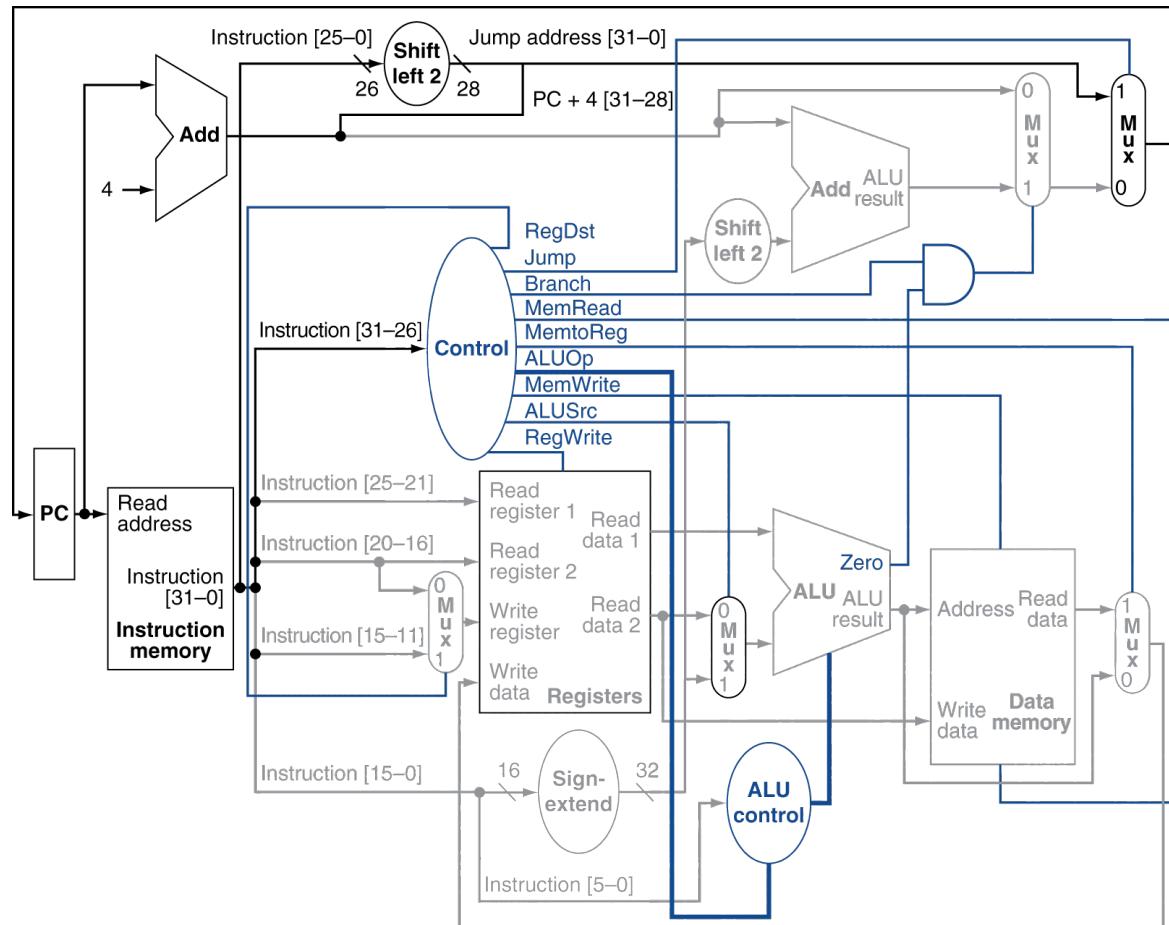


The Processor


Designing the datapath



Program Execution (performance)

- Algorithm
 - Determines **number of operations** executed
- Programming language, compiler, architecture (Instruction Set Architecture – ISA)
 - Determine number of **machine instructions** executed **per operation** (clock Cycles Per Instruction – CPI)
- Processor and memory system
 - Determine **how fast instructions** are **executed** (cycle time)
- I/O system (and OS)
 - Determines **how fast I/O operations** are **executed**

Program Execution

 

32 bit MIPS R3000 processor (115000 transistors) early 1990s

- We will examine two MIPS hardware implementations (aka “datapath”) with identical ISAs:
 - A simplified version
 - A more realistic pipelined version (Instruction-Level Parallelism)
- We will subsequently introduce “exception” handling and what this requires in the datapath
- Simple (but sufficient) subset, only essential instructions
Different types of instructions (Instruction Set):
 - Memory access: `lw`, `sw`
 - Arithmetic/logical: `add`, `sub`, `and`, `or`, `slt`
 - Control transfer: `beq`, `j`

Böhm – Jacopini theorem

The “structured program” theorem (from programming language theory):


Böhm, Corrado and Jacopini, Giuseppe (1966).

“Flow Diagrams, Turing Machines and Languages with only Two Formation Rules”. Communications of the ACM 9(5):366-371.


<http://www.cs.unibo.it/~martini/PP/bohm-jac.pdf>

A class of control flow graphs can compute any computable function (algorithm) if it combines subprograms in only three specific ways (*i.e.*, by means of only three control structures):

 1) Executing one subprogram, and then another subprogram (sequence)



 2) Executing one of two subprograms according to the value of a Boolean expression (selection)




3) Repeatedly executing a subprogram as long as a Boolean expression is true (iteration)

Note: assembly/machine code is not “structured” HLL (as it uses **Go To**).

Edsger Dijkstra (1968).

“**Go To** Statement Considered Harmful”. Communications of the ACM. 11 (3): 147–148.
 
<https://homepages.cwi.nl/~storm/teaching/reader/Dijkstra68.pdf>



Frank Rubin (1987).

“GOTO Considered Harmful” Considered Harmful. Communications of the ACM. 30 (3): 195–196.

<http://www.ecn.purdue.edu/ParaMount/papers/rubin87goto.pdf>

“GOTO Considered Harmful” Considered Harmful’ Considered Harmful?” ...

Instruction Set Architecture (ISA)

Special Architectures:

- (Super) vector computers
- GPU (matrix operations)
- Special purpose (signal processing, ECU, ...)

Instruction Set Architecture (ISA)

Design Principles (HW/SW):

1. Regularity
2. Smaller is Faster
3. Make the Common Case Fast
4. Good Design demands Good Compromises

Instruction Set Architecture (ISA)

Different instruction **types**:

Memory access: lw, sw
Arithmetic/logical: add, sub, and, or, slt
Control transfer: beq, j

Different instruction **instances**:

add \$s1, \$s2, \$s3
add \$s1, \$s1, \$s2
add \$s1, \$s1, \$s1

Different instruction (encoding) **formats**:

Name	Fields						Comments
Field size	6 bits	5 bits	5 bits	5 bits	5 bits	6 bits	All MIPS instructions are 32 bits long
R-format	op	rs	rt	rd	shamt	funct	Arithmetic instruction format
I-format	op	rs	rt	address/immediate			Transfer, branch, imm. format
J-format	op	target address					Jump instruction format


Logic Design Basics (recap)

- Information encoded in **binary digits**
 - Low voltage = 0, High voltage = 1 (or reverse)
 - One wire per bit
 - Multi-bit data encoded on multi-wire **buses**
- **Combinational** element
 - **Operate** on **data**
 - Output is a **function** of input
- **State (sequential)** elements
 - **Store/Hold/Retrieve** information

Combinational Elements


- AND-gate

- $Y = A \& B$

 


- Multiplexer

- $Y = S ? I1 : I0$

 


- Adder

- $Y = A + B$

 

- Arithmetic/Logic Unit



- $Y = F(A, B)$

 

Sequential Elements

Register: stores data in a memory circuit

 
 
- Uses a clock signal Clk to determine **when** to **update** the **stored** value Q with D
- (rising/falling) **Edge-triggered**: **update** data in memory **when** Clk changes (from 0 to 1/1 to 0)



Sequential Elements

Register with **write control**

 
 
- Only updates on **clock edge** only when **write control input is 1**
- Used when stored value is to be kept over **multiple** clock cycles



Clocking Methodology

Combinational logic transforms data **during** clock cycles

  - Between clock edges
- Input from state elements,
Output to state element
- **Longest delay** due to combinational logic (implementing ISA “instructions”) determines **minimum** required **clock period**



Executing Machine Instructions

```
1      .data
2
3  values: .word 10
4          .word 12
5  result: .word 9
6
7      .text
8  start:
9
10 # ALU operations
11     li  $t1, 1
12     li  $t2, 2
13     add $t3, $t1, $t2
14
15 # memory operations
16     la  $t0, values
17     lw  $t1, 0($t0)
18     lw  $t2, 4($t0)
19     add $t3, $t1, $t2
20     la  $t0, result
21     sw  $t3, 0($t0)
22
23 # control flow
24     beq $t3, $t3, start
25     addi $t3, $t3, 2
26
27     j   start
```

Executing Machine Instructions

Registers		Coproc 1	Coproc 0
Name	Number		Value
\$zero	0		0x00000000
\$at	1		0x00000000
\$v0	2		0x00000000
\$v1	3		0x00000000
\$a0	4		0x00000000
\$a1	5		0x00000000
\$a2	6		0x00000000
\$a3	7		0x00000000
\$t0	8		0x00000000
\$t1	9		0x00000000
\$t2	10		0x00000000
\$t3	11		0x00000000
\$t4	12		0x00000000
\$t5	13		0x00000000
\$t6	14		0x00000000
\$t7	15		0x00000000
\$s0	16		0x00000000
\$s1	17		0x00000000
\$s2	18		0x00000000
\$s3	19		0x00000000
\$s4	20		0x00000000
\$s5	21		0x00000000
\$s6	22		0x00000000
\$s7	23		0x00000000
\$t8	24		0x00000000
\$t9	25		0x00000000
\$k0	26		0x00000000
\$k1	27		0x00000000
\$gp	28		0x10008000
\$sp	29		0x7ffffc
\$fp	30		0x00000000
\$ra	31		0x00000000
pc			0x00400000
hi			0x00000000
lo			0x00000000


Executing Machine Instructions

Text Segment					
Bkpt	Address	Code	Basic		Source
<input type="checkbox"/>	0x00400000	0x24090001	addiu \$9,\$0,0x00000001	11:	li \$t1, 1
<input type="checkbox"/>	0x00400004	0x240a0002	addiu \$10,\$0,0x0000...	12:	li \$t2, 2
<input type="checkbox"/>	0x00400008	0x012a5820	add \$11,\$9,\$10	13:	add \$t3, \$t1, \$t2
<input type="checkbox"/>	0x0040000c	0x3c011001	lui \$1,0x00001001	16:	la \$t0, values
<input type="checkbox"/>	0x00400010	0x34280000	ori \$8,\$1,0x00000000		
<input type="checkbox"/>	0x00400014	0x8d090000	lw \$9,0x00000000(\$8)	17:	lw \$t1, 0(\$t0)
<input type="checkbox"/>	0x00400018	0x8d0a0004	lw \$10,0x00000004(\$8)	18:	lw \$t2, 4(\$t0)
<input type="checkbox"/>	0x0040001c	0x012a5820	add \$11,\$9,\$10	19:	add \$t3, \$t1, \$t2
<input type="checkbox"/>	0x00400020	0x3c011001	lui \$1,0x00001001	20:	la \$t0, result
<input type="checkbox"/>	0x00400024	0x34280008	ori \$8,\$1,0x00000008		
<input type="checkbox"/>	0x00400028	0xad0b0000	sw \$11,0x00000000(\$8)	21:	sw \$t3, 0(\$t0)
<input type="checkbox"/>	0x0040002c	0x116bfff4	beq \$11,\$11,0xffffffff4	24:	beq \$t3, \$t3, start
<input type="checkbox"/>	0x00400030	0x216b0002	addi \$11,\$11,0x0000...	25:	addi \$t3, \$t3, 2
<input type="checkbox"/>	0x00400034	0x08100000	j 0x00400000	27:	j start


Instruction Execution

- **PC** → instruction memory, **fetch** instruction
- Register numbers → **register file**, **read** registers
- Depending on **instruction type (class)**
 - Use **ALU** to calculate
 - Arithmetic result
 - Memory address for load/store
 - Branch target address
 - Access data **memory** for load/store
 - **PC** ← **PC + 4** (“next sequential instruction”) or **target address**


CPU Overview

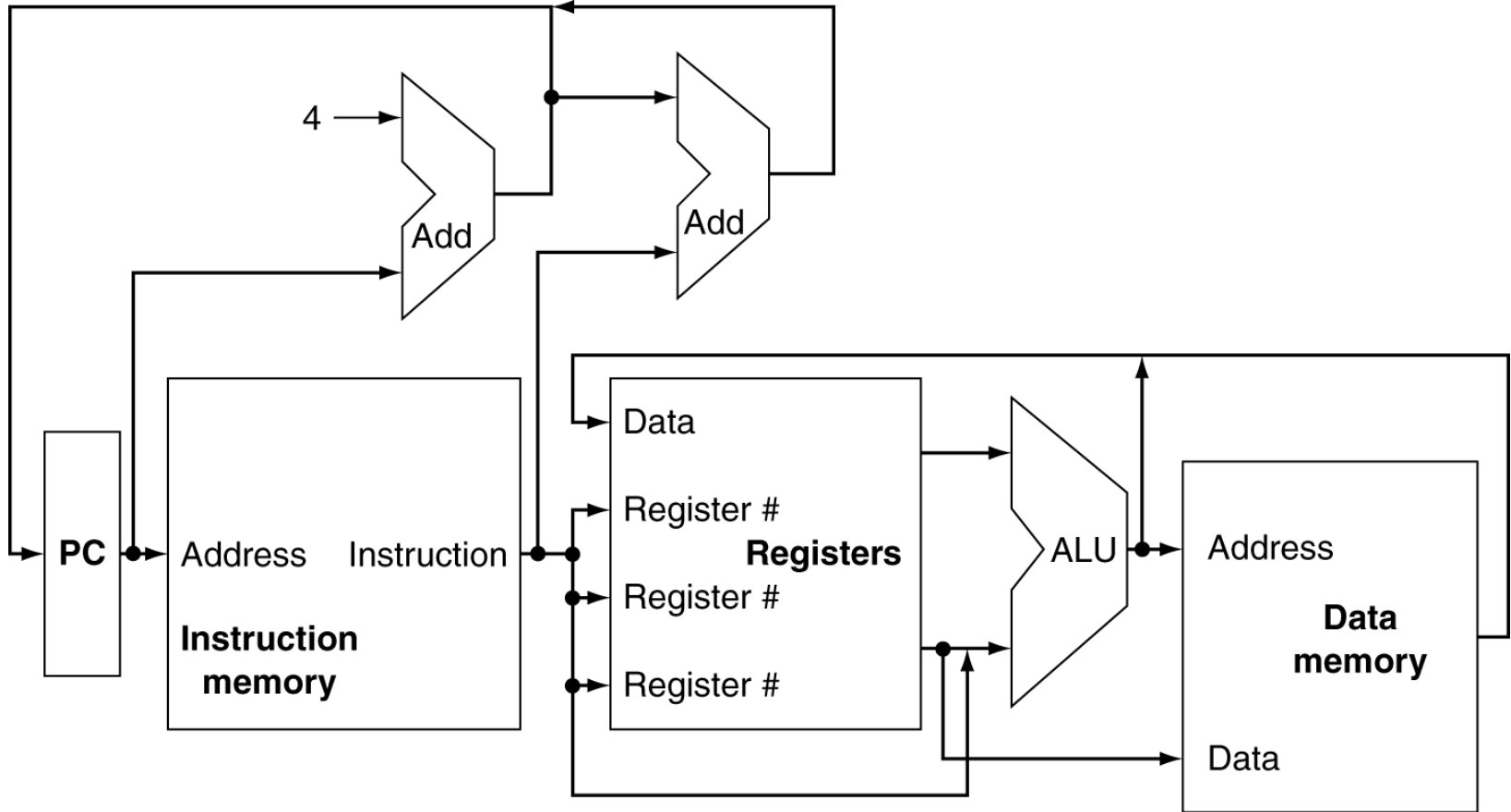

Multiplexers

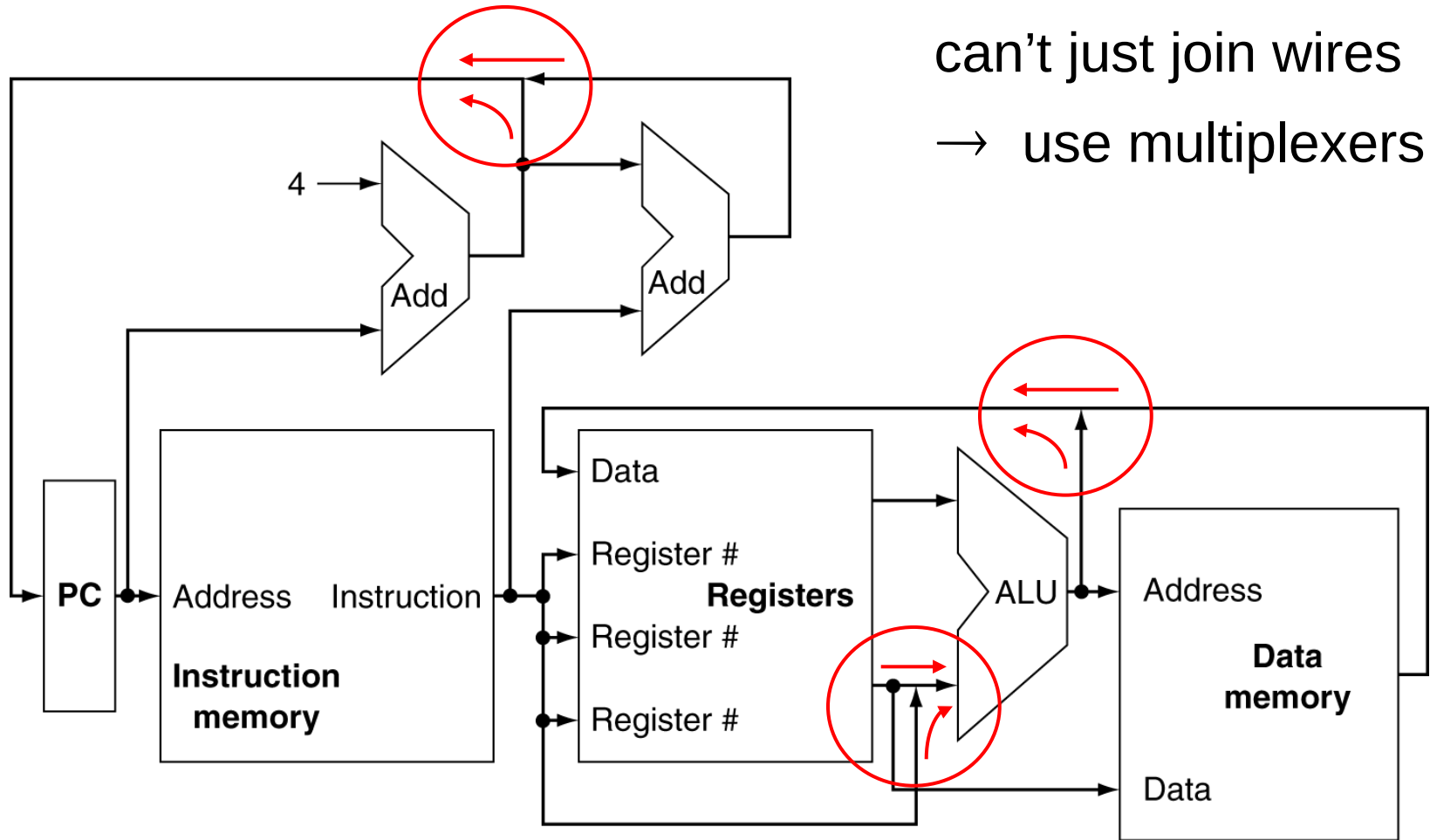

Control

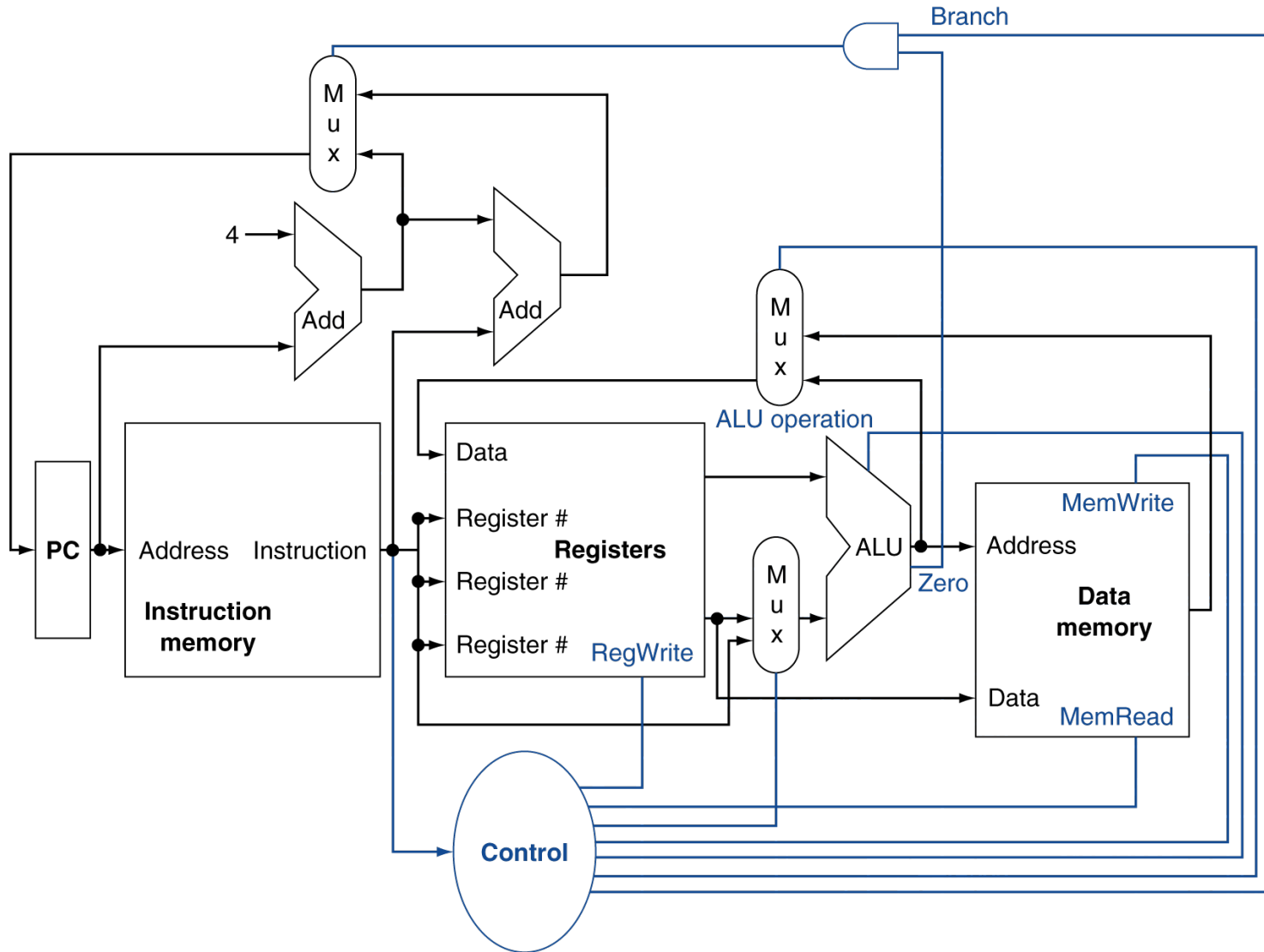

Building a Datapath



- Datapath =
 - CPU **hardware architecture** that processes **instructions** and **data**
 - registers, ALUs, multiplexers, memories
- We will build a simplified MIPS datapath incrementally, refining the overview design

Instruction Fetch

WORD ALIGNED (x 4)

INSTRUCTION MEMORY (.text)
  
$$\begin{array}{r} 116 \\ +1 \\ \hline 117 \end{array}$$
 MODULO



PC




UNSIGNED INTEGER


$PC \leftarrow PC + 4$



Program Counter (PC) is unsigned

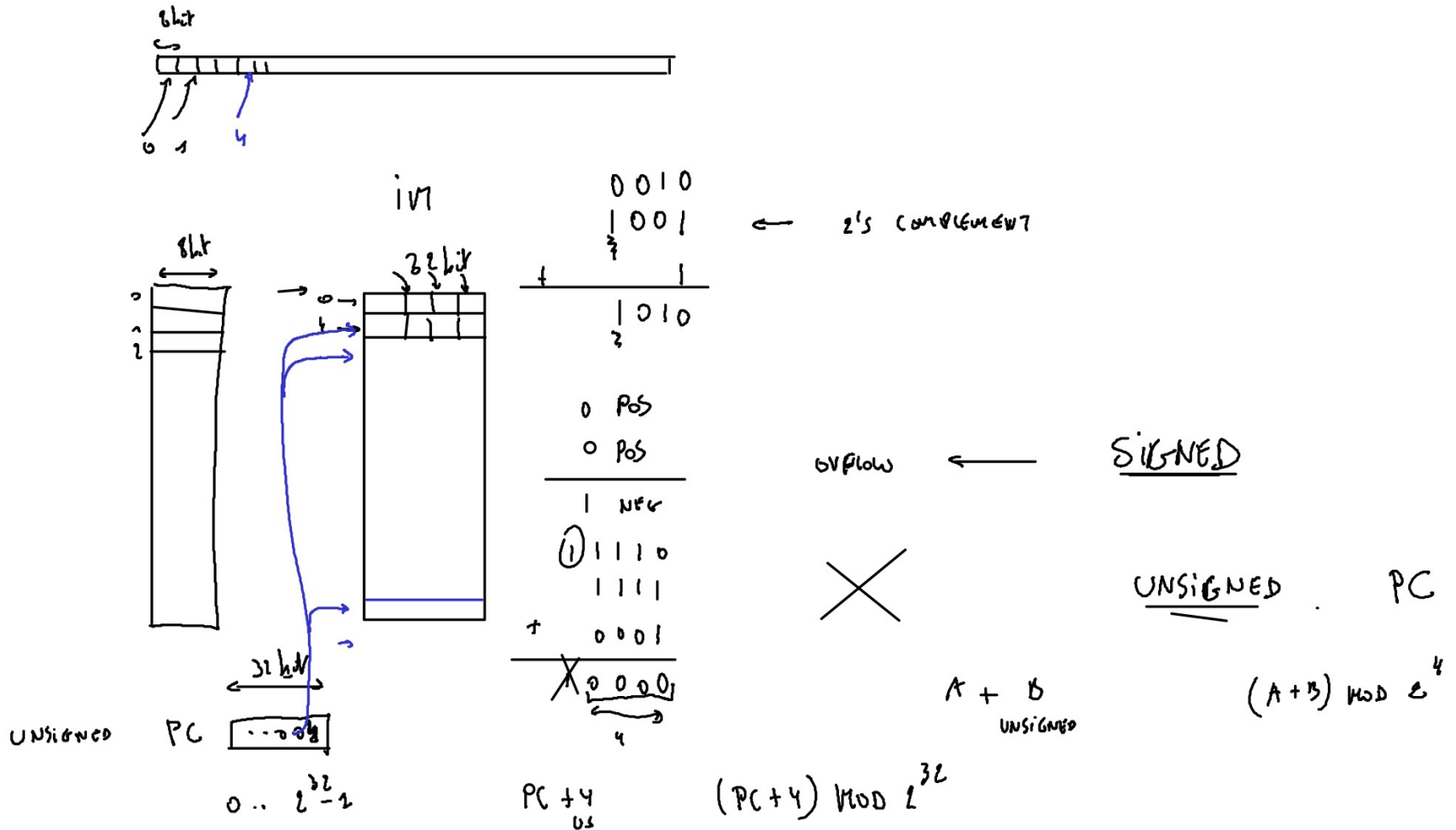


Instruction Fetch

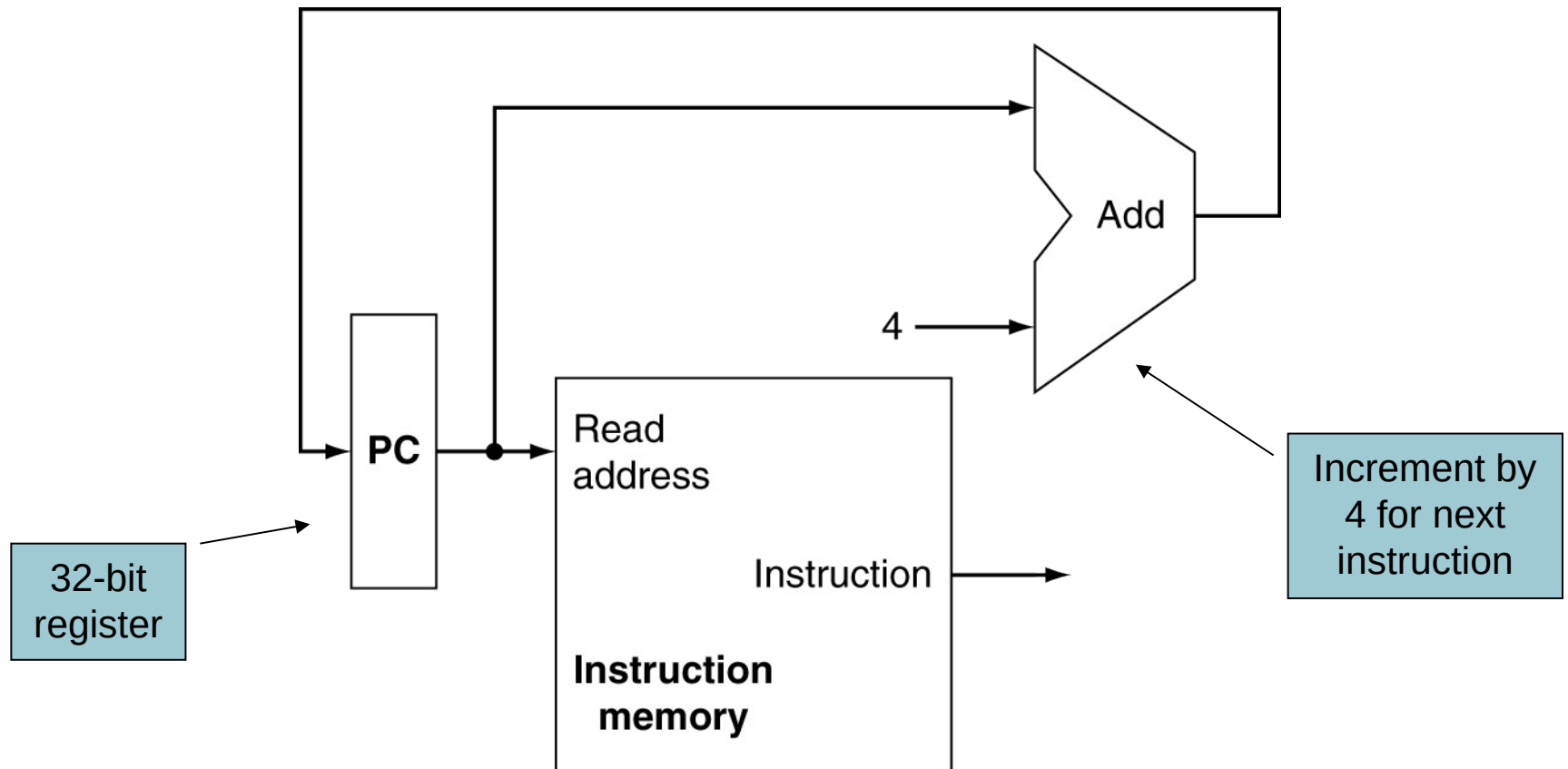

R-Format Instructions

Name	Fields						Comments
Field size	6 bits	5 bits	5 bits	5 bits	5 bits	6 bits	All MIPS instructions are 32 bits long
R-format	op	rs	rt	rd	shamt	funct	Arithmetic instruction format
I-format	op	rs	rt	address/immediate			Transfer, branch, imm. format
J-format	op	target address					Jump instruction format

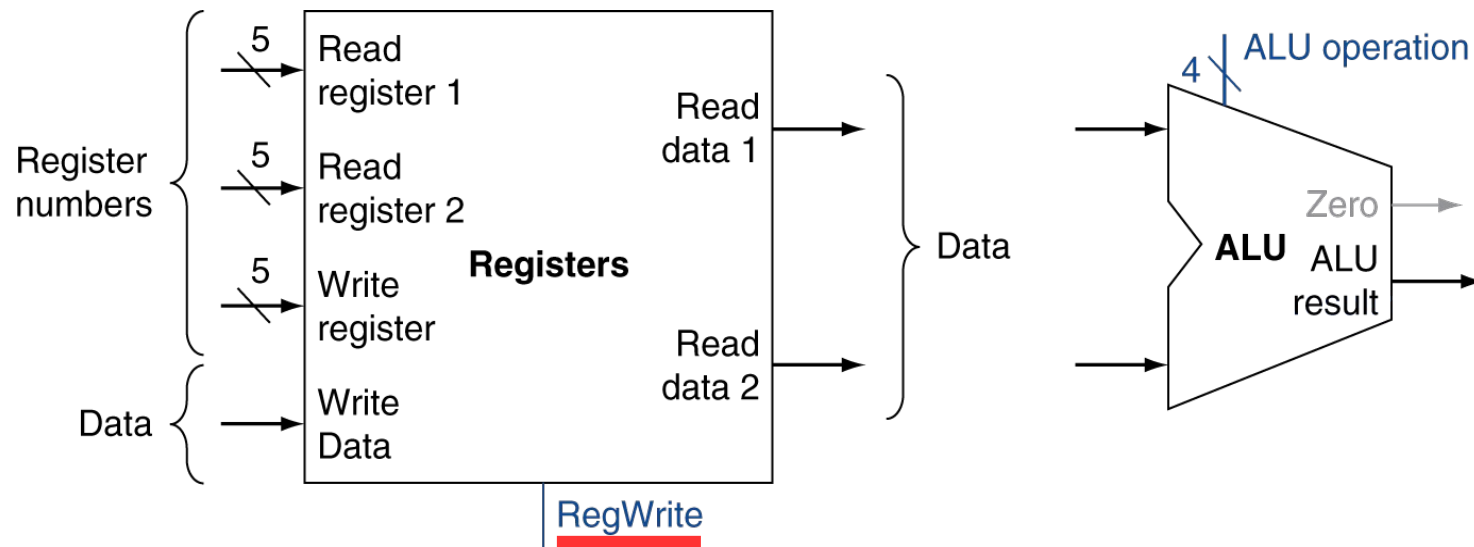- Read two register operands
- Perform arithmetic/logical operation
- Write register result




a. Registers

b. ALU

Load/Store Instructions

Name	Fields						Comments
Field size	6 bits	5 bits	5 bits	5 bits	5 bits	6 bits	All MIPS instructions are 32 bits long
R-format	op	rs	rt	rd	shamt	funct	Arithmetic instruction format
I-format	op	rs	rt	address/immediate			Transfer, branch, imm. format
J-format	op	target address					Jump instruction format

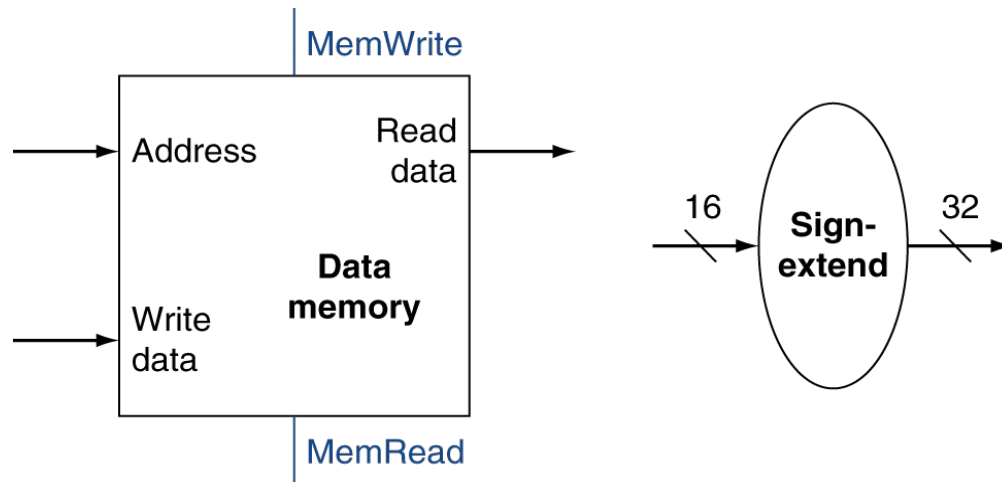
- Read register operands
- Calculate address using 16-bit offset
 - use ALU, but sign-extend offset
- Load: Read memory and update register
- Store: Write register value to memory



a. Data memory unit

b. Sign extension unit

R-Type/Load/Store Datapath

 


Branch Instructions

Name	Fields						Comments
Field size	6 bits	5 bits	5 bits	5 bits	5 bits	6 bits	All MIPS instructions are 32 bits long
R-format	op	rs	rt	rd	shamt	funct	Arithmetic instruction format
I-format	op	rs	rt	address/immediate			Transfer, branch, imm. format
J-format	op	target address					Jump instruction format

- Read register operands
- Compare operands
 - Use ALU, subtract and check Zero output
- Calculate target address
 - Sign-extend displacement
 - Shift left 2 places
(instructions are word-aligned)
 - Add to PC + 4
 - Already calculated by instruction fetch


Branch Instructions

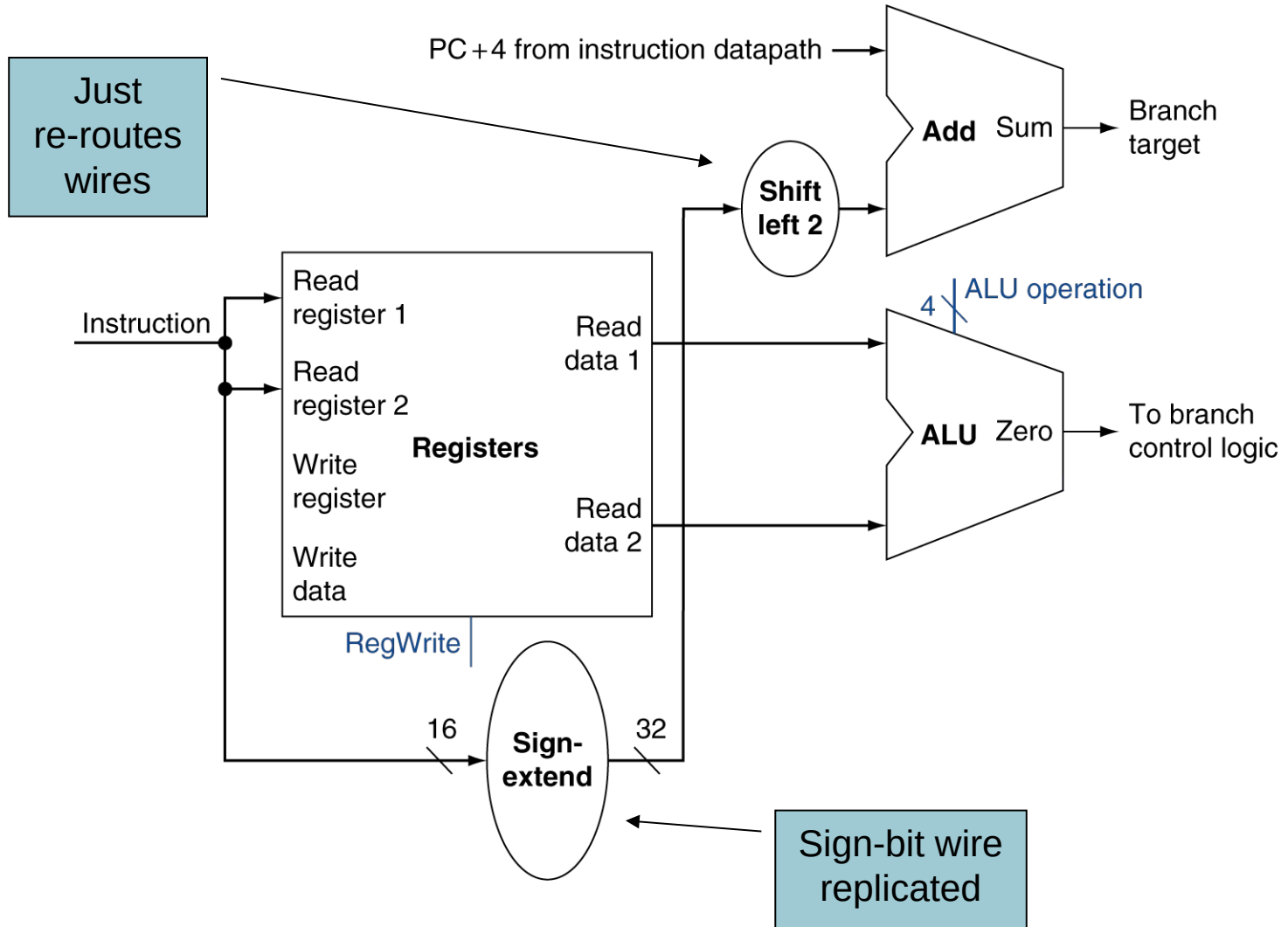

Composing the Elements

- First attempt at datapath processes one **instruction in one clock cycle**
 - Each datapath element can only do one function at a time (*i.e.*, in one clock cycle)
 - Hence, we need **separate** instruction and data memories!
- Use **multiplexers** where **alternate data sources** (*e.g.*, from ALU or from memory) are used for different instructions

Full Datapath

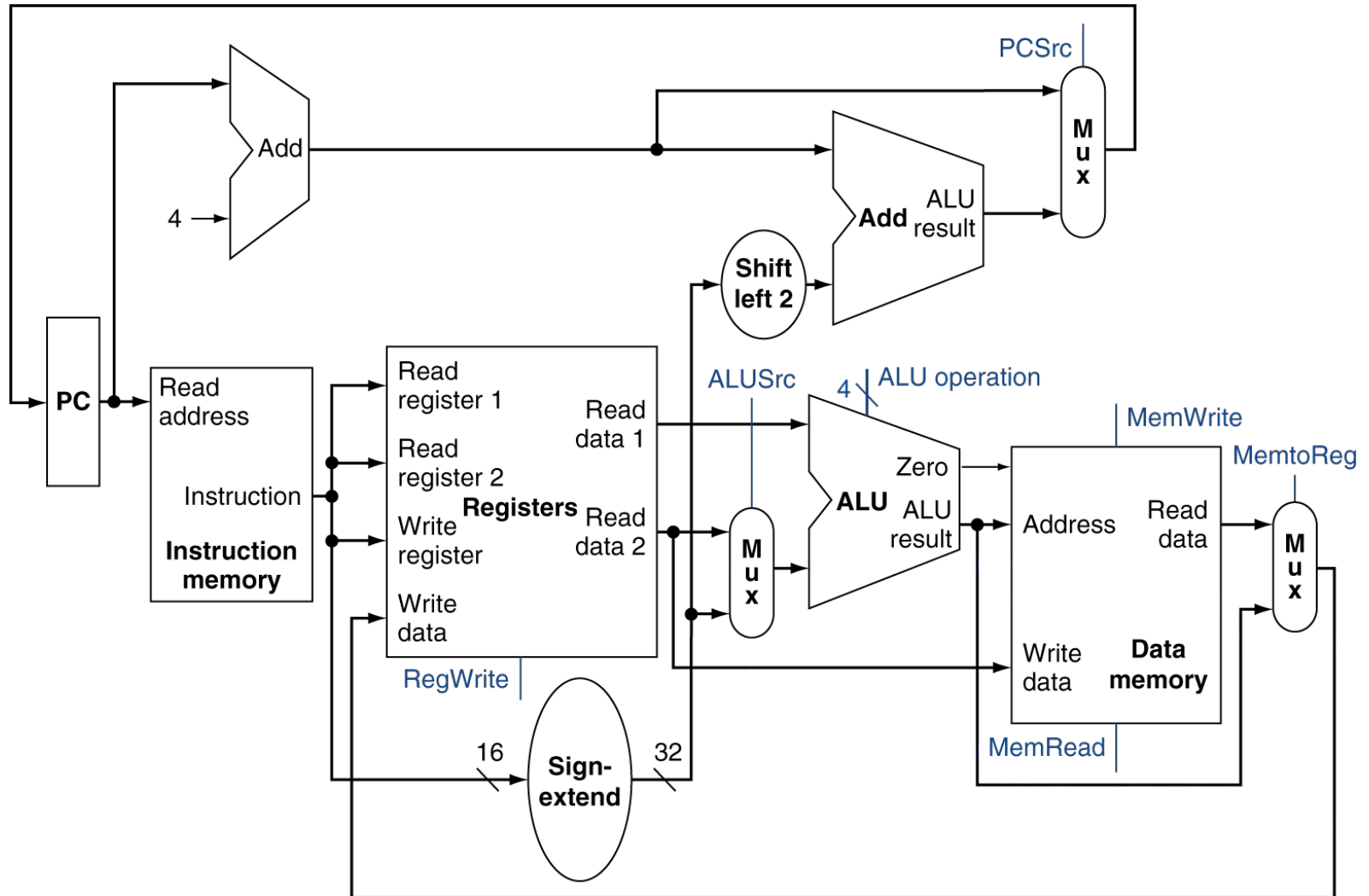



ALU Control

- ALU used for
 - R-type: Function depends on `funct` field
 - Load/Store: Function = **add**
 - Branch `beq`: Function = **subtract**

ALU control	Function
0000	AND
0001	OR
0010	add
0110	subtract
0111	set-on-less-than
1100	NOR

ALU Control

- 2-bit ALUOp derived from opcode

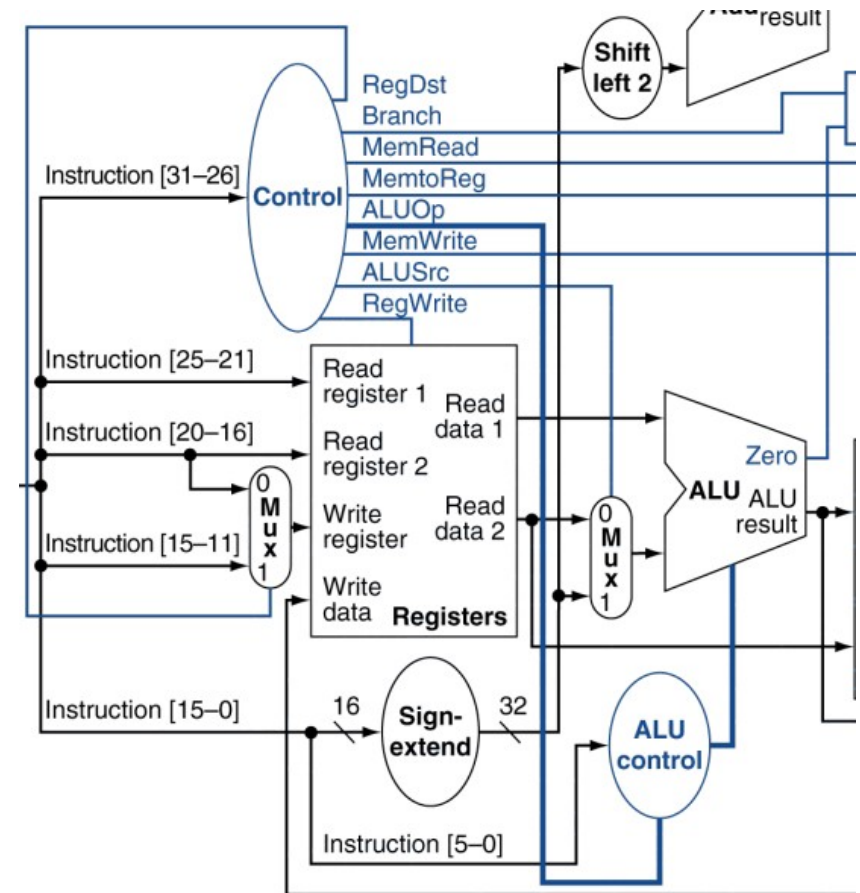 


ALU Control

- 2-bit ALUOp derived from opcode
- Combinational logic for ALU control


opcode	ALUOp	Operation	funct	ALU function	ALU control
lw	00	load word	XXXXXX	add	0010
sw	00	store word	XXXXXX	add	0010
beq	01	branch equal	XXXXXX	subtract	0110
R-type	10	add	100000	add	0010
		subtract	100010	subtract	0110
		AND	100100	AND	0000
		OR	100101	OR	0001
		set-on-less-than	101010	set-on-less-than	0111

The Main Control Unit

- information extracted from instruction

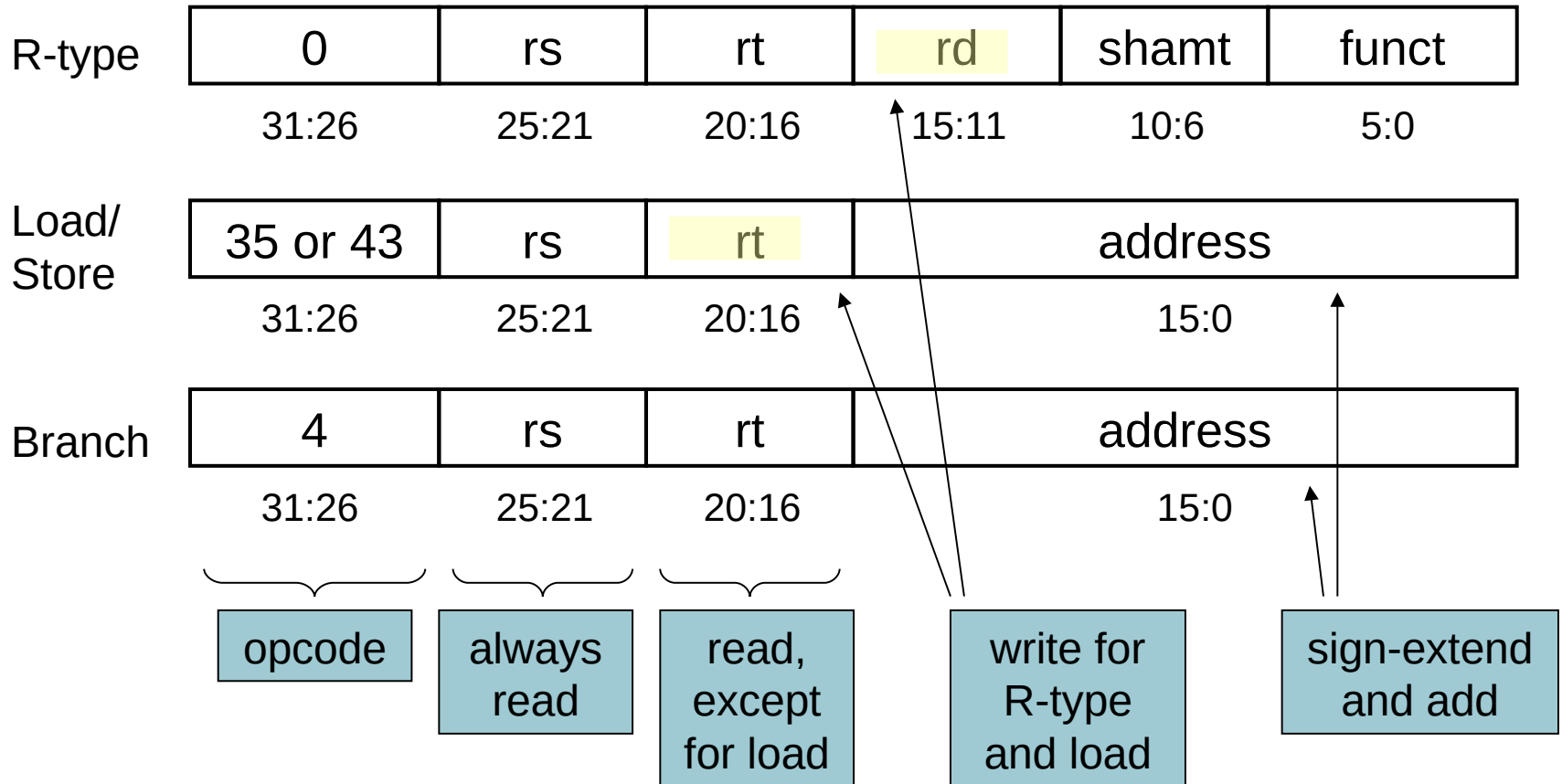


Datapath With Control

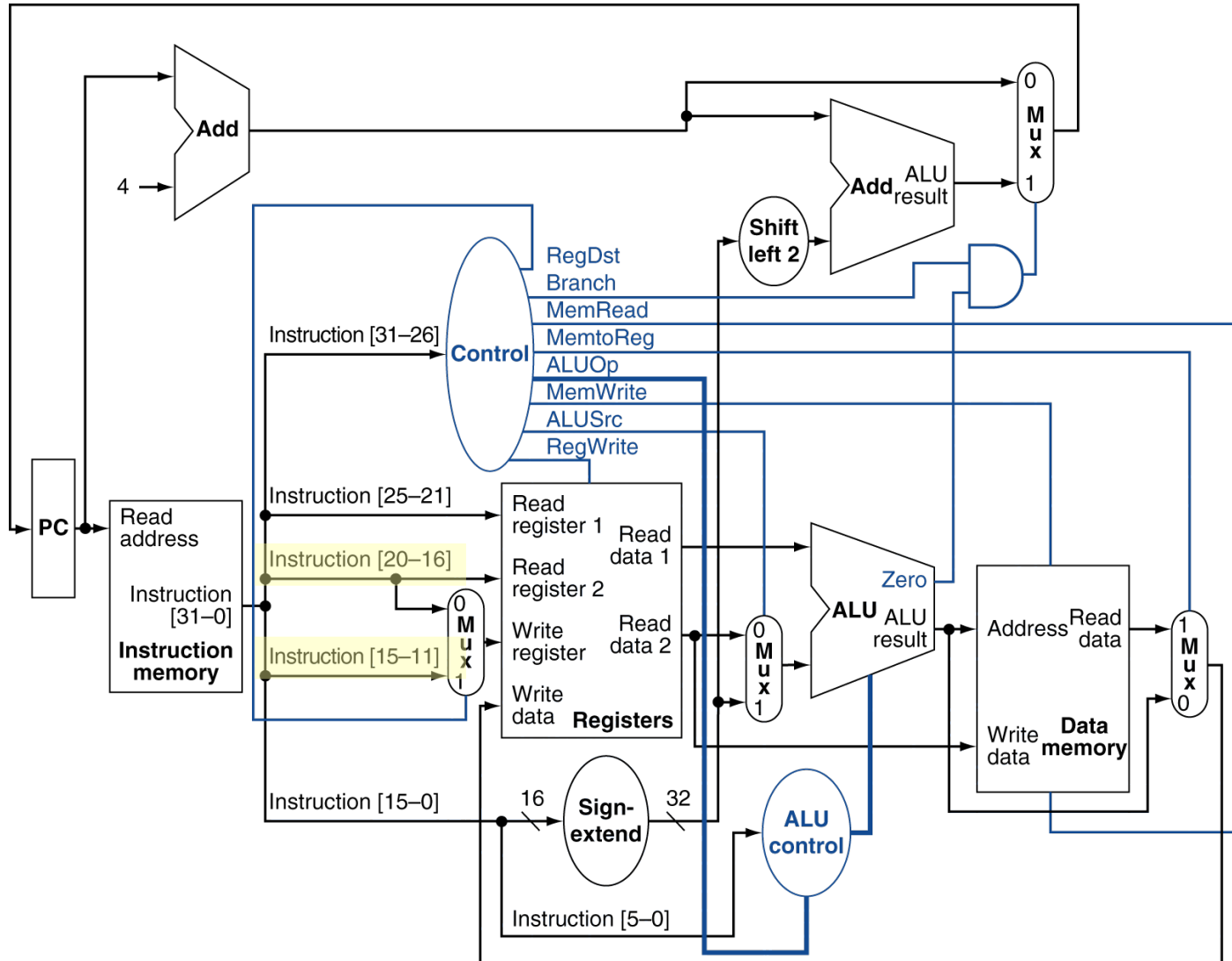

Example program

```
1      .data
2
3  values: .word    10
4          .word    12
5  result: .word    9
6
7      .text
8  start:
9
10     # ALU operations
11     li    $t1, 1
12     li    $t2, 2
13     add   $t3, $t1, $t2
14
15     # memory operations
16     la    $t0, values
17     lw    $t1, 0($t0)
18     lw    $t2, 4($t0)
19     add   $t3, $t1, $t2
20     la    $t0, result
21     sw    $t3, 0($t0)
22
23     # control flow
24     beq   $t3, $t3, start
25     addi  $t3, $t3, 2
26
27     j     start
```


R-Type Instruction

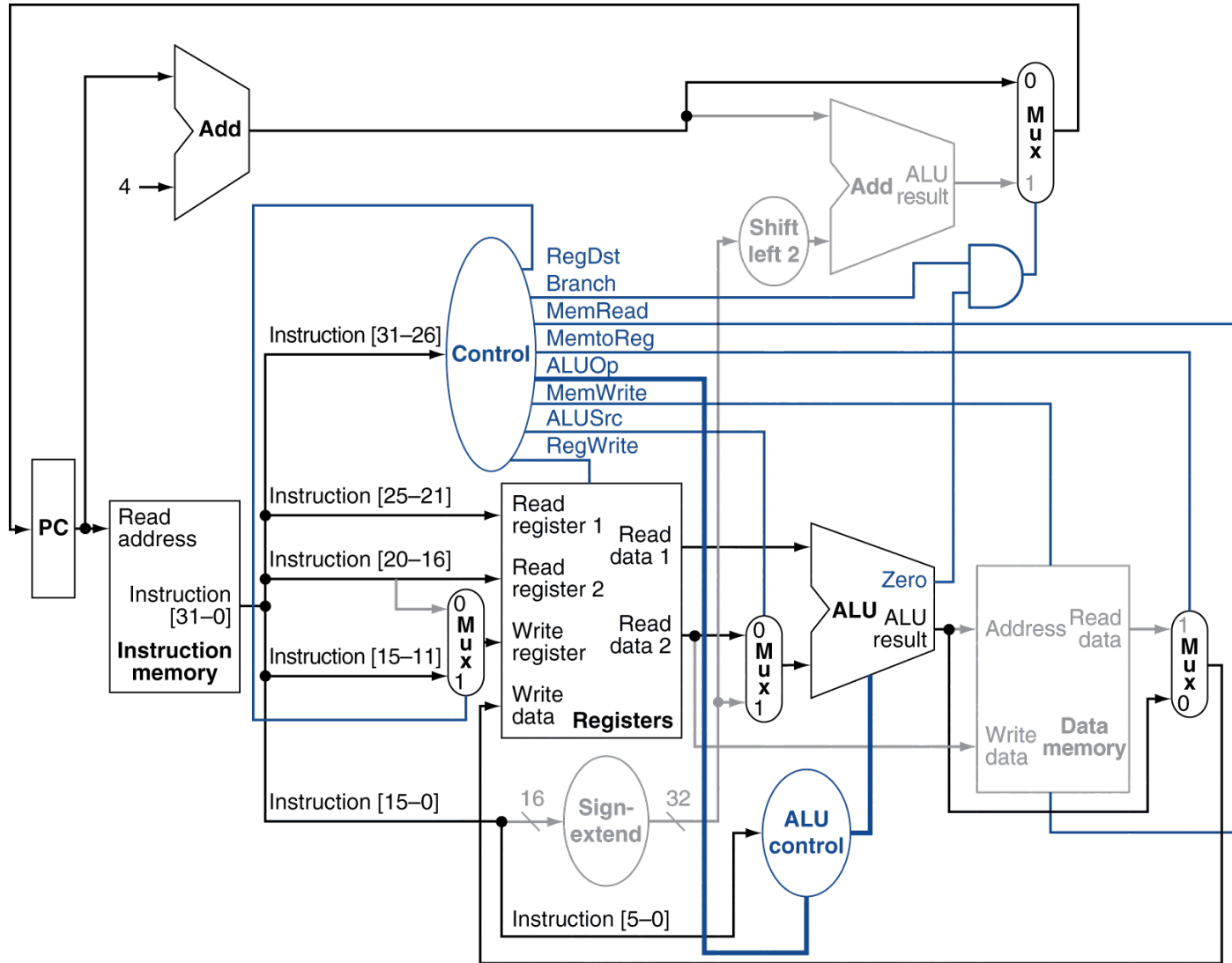

0x0040001c	0x012a5820	add \$11,\$9,\$10	19:	add \$t3, \$t1, \$t2
------------	------------	-------------------	-----	----------------------

R-Type Instruction encoding

0x0040001c	0x012a5820	add \$t1,\$t1,\$t2	19:	add \$t3, \$t1, \$t2
------------	------------	--------------------	-----	----------------------

MIPS Reference Data

①



CORE INSTRUCTION SET

NAME, MNEMONIC	FOR-MAT	OPERATION (in Verilog)	OPCODE / FUNCT (Hex)
Add	add	R R[rd] = R[rs] + R[rt]	(1) 0 / 20 _{hex}
Add Immediate	addi	I R[rt] = R[rs] + SignExtImm	(1,2) 8 _{hex}
Add Imm. Unsigned	addiu	I R[rt] = R[rs] + SignExtImm	(2) 9 _{hex}
Add Unsigned	addu	R R[rd] = R[rs] + R[rt]	0 / 21 _{hex}
And	and	R R[rd] = R[rs] & R[rt]	0 / 24 _{hex}
And Immediate	andi	I R[rt] = R[rs] & ZeroExtImm	(3) c _{hex}
Branch On Equal	beq	I if(R[rs]==R[rt]) PC=PC+4+BranchAddr	(4) 4 _{hex}

add opcode = 00₁₆ = 000000₂
 add func = 20₁₆ = 100000₂
 add shamt = 00₁₆ = 00000₂
 \$t1 = \$9 = 01001₂
 \$t2 = \$10 = 01010₂
 \$t3 = \$11 = 01011₂

(1) May cause overflow exception

(2) SignExtImm = { 16{immediate[15]}, immediate }

(3) ZeroExtImm = { 16{1b'0}, immediate }

(4) BranchAddr = { 14{immediate[15]}, immediate, 2'b0 }

(5) JumpAddr = { PC+4[31:28], address, 2'b0 }

(6) Operands considered unsigned numbers (vs. 2's comp.)

(7) Atomic test&set pair; R[rt] = 1 if pair atomic, 0 if not atomic

encoding of add \$t3, \$t1, \$t2

= 000000 01001 01010 01011 00000 100000₂

= 0000 0001 0010 1010 0101 1000 0010 0000₂

= 0 1 2 a 5 8 2 0₁₆

BASIC INSTRUCTION FORMATS

R	opcode	rs	rt	rd	shamt	funct
	31	26 25	21 20	16 15	11 10	6 5
	0					
I	opcode	rs	rt	immediate		
	31	26 25	21 20	16 15		
	0					
J	opcode	address				
	31	26 25				
	0					

Load Instruction

LW

REG #
□ ,

OFFSET (BASE REG #)
7/16 bit
CONTENT


15
BASE ADDRESS

DATA MEM


$[-2^{15} \dots +2^{15}-1]$

32 x 1024

Load Instruction

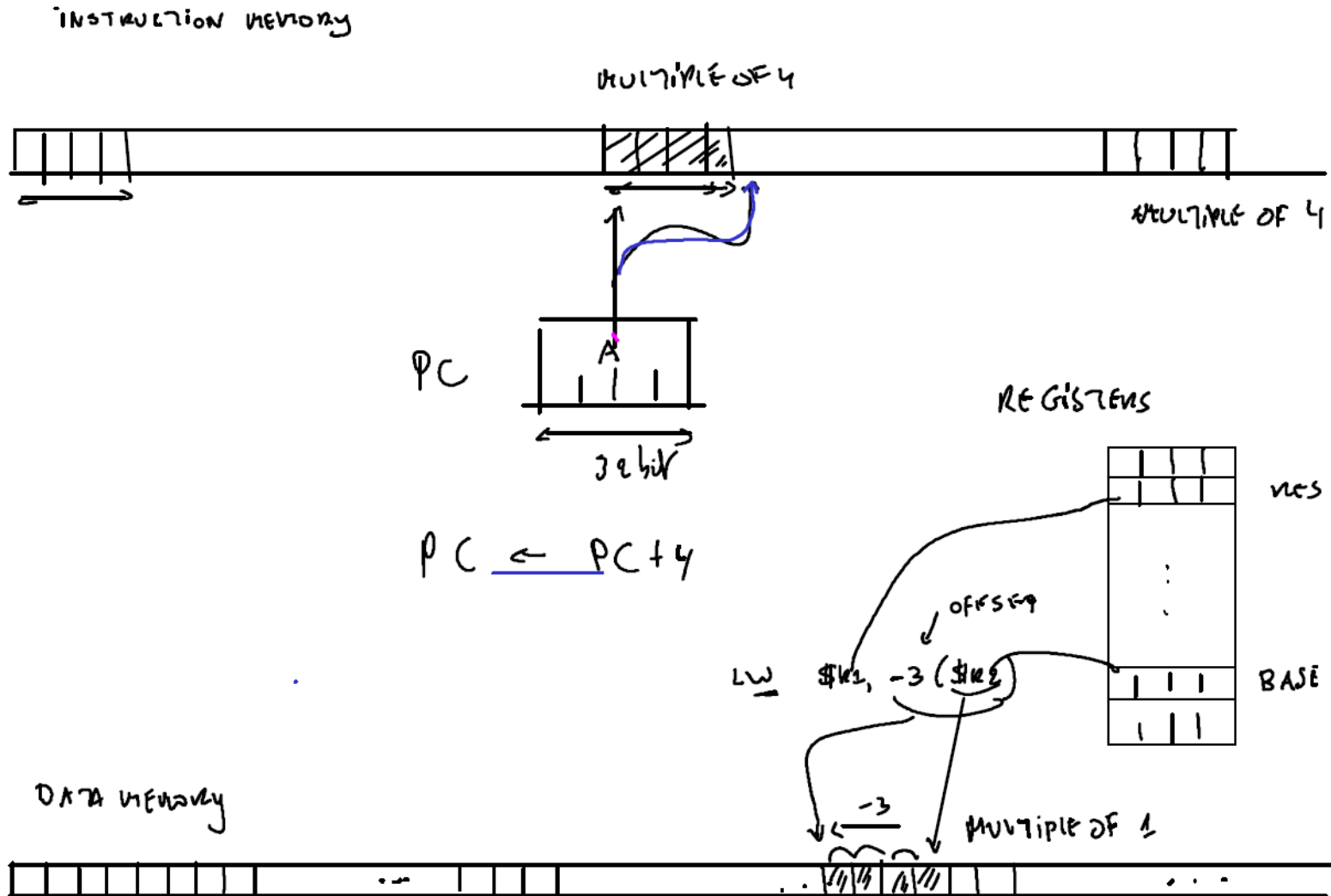

Load Instruction

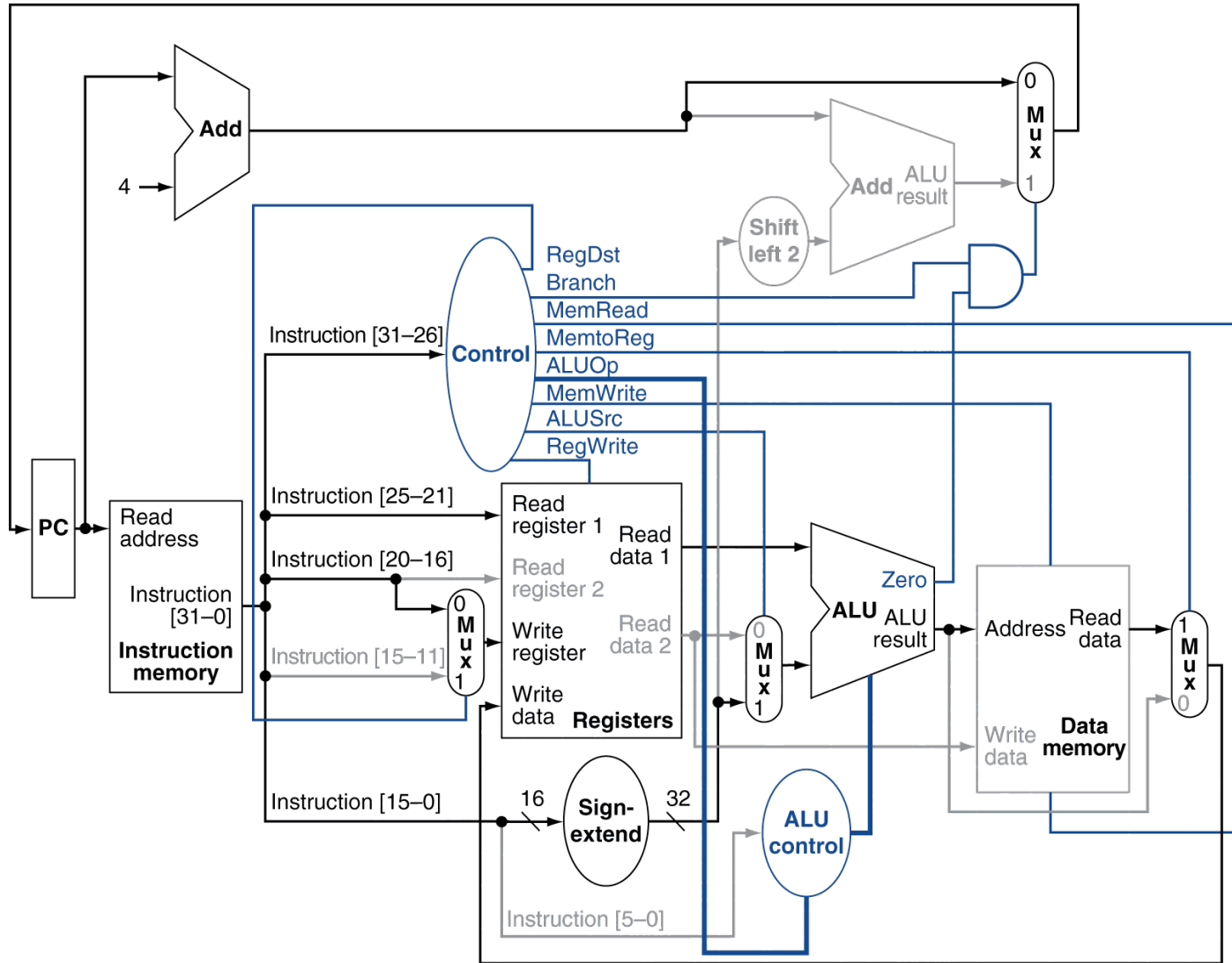

```
0x00400018 0x8d0a0004 lw $t0,0x00000004($8) 18: lw $t2, 4($t0)
```

Load Instruction encoding

```
0x00400018 0x8d0a0004 lw $t0,0x00000004($8) 18: lw $t2, 4($t0)
```

MIPS Reference Data

①



CORE INSTRUCTION SET			OPCODE / FUNCT (Hex)
NAME, MNEMONIC	FOR-MAT	OPERATION (in Verilog)	
Add	add	R R[rd] = R[rs] + R[rt]	(1) 0/20 _{hex}
Add Immediate	addi	I R[rt] = R[rs] + SignExtImm	(1,2) 8 _{hex}
Add Imm. Unsigned	addiu	I R[rt] = R[rs] + SignExtImm	(2) 9 _{hex}
Add Unsigned	addu	R R[rd] = R[rs] + R[rt]	0/21 _{hex}
And	and	R R[rd] = R[rs] & R[rt]	0/24 _{hex}
And Immediate	andi	I R[rt] = R[rs] & ZeroExtImm	(3) c _{hex}
Branch On Equal	beq	I if(R[rs]==R[rt]) PC=PC+4+BranchAddr	(4) 4 _{hex}
Branch On Not Equal	bne	I if(R[rs]!=R[rt]) PC=PC+4+BranchAddr	(4) 5 _{hex}
Jump	j	J PC=JumpAddr	(5) 2 _{hex}
Jump And Link	jal	J R[31]=PC+8;PC=JumpAddr	(5) 3 _{hex}
Jump Register	jr	R PC=R[rs]	0/08 _{hex}
Load Byte Unsigned	lbu	I R[rt]={24'b0,M[R[rs] +SignExtImm](7:0)}	(2) 24 _{hex}
Load Halfword Unsigned	lhu	I R[rt]={16'b0,M[R[rs] +SignExtImm](15:0)}	(2) 25 _{hex}
Load Linked	ll	I R[rt] = M[R[rs]+SignExtImm]	(2,7) 30 _{hex}
Load Upper Imm.	lui	I R[rt] = {imm, 16'b0}	f _{hex}
Load Word	lw	I R[rt] = M[R[rs]+SignExtImm]	(2) 23 _{hex}


lw opcode = 23₁₆ = 100011₂
 \$t0 = \$8 = 01000₂
 \$t2 = \$10 = 01010₂
 4 = 0000 0000 0000 0100₂

encoding of lw \$t2, 4(\$t0)

= 100011 01000 01010 0000 0000 0000 0100₂
 = 1000 1101 0000 1010 0000 0000 0000 0100₂
 = 8 d 0 a 0 0 0 4₁₆

- (1) May cause overflow exception
- (2) SignExtImm = { 16{immediate[15]}, immediate }
- (3) ZeroExtImm = { 16{1b'0'}, immediate }
- (4) BranchAddr = { 14{immediate[15]}, immediate, 2'b0 }
- (5) JumpAddr = { PC+4[31:28], address, 2'b0 }
- (6) Operands considered unsigned numbers (vs. 2's comp.)
- (7) Atomic test&set pair; R[rt] = 1 if pair atomic, 0 if not atomic



BASIC INSTRUCTION FORMATS

 


Branch-on-Equal Instruction

INSTRUCTION MEMORY

MULTIPLE OF 4

  

Branch-on-Equal Instruction

 

0x0040002c 0x116bfff4|beq \$t1,\$t1,0xffffffff|24: beq \$t3, \$t3, start

beq Instruction encoding

0x0040002c | 0x116bfff4 | beq \$11,\$11,0xffffffff4 | 24: beq \$t3, \$t3, start

Text Segment				
Bkpt	Address	Code	Basic	Source
<input type="checkbox"/>	0x00400000	0x24090001	addiu \$9,\$0,0x00000001	11: li \$t1, 1
<input type="checkbox"/>	0x00400004	0x240a0002	addiu \$10,\$0,0x0000...	12: li \$t2, 2
<input type="checkbox"/>	0x00400008	0x012a5820	add \$11,\$9,\$10	13: add \$t3, \$t1, \$t2
<input type="checkbox"/>	0x0040000c	0x3c011001	lui \$1,0x00001001	16: la \$t0, values
<input type="checkbox"/>	0x00400010	0x34280000	ori \$8,\$1,0x00000000	
<input type="checkbox"/>	0x00400014	0x8d090000	lw \$9,0x00000000(\$8)	17: lw \$t1, 0(\$t0)
<input type="checkbox"/>	0x00400018	0x8d0a0004	lw \$10,0x00000004(\$8)	18: lw \$t2, 4(\$t0)
<input type="checkbox"/>	0x0040001c	0x012a5820	add \$11,\$9,\$10	19: add \$t3, \$t1, \$t2
<input type="checkbox"/>	0x00400020	0x3c011001	lui \$1,0x00001001	20: la \$t0, result
<input type="checkbox"/>	0x00400024	0x34280008	ori \$8,\$1,0x00000008	
<input type="checkbox"/>	0x00400028	0xad0b0000	sw \$11,0x00000000(\$8)	21: sw \$t3, 0(\$t0)
<input type="checkbox"/>	0x0040002c	0x116bfff4	beq \$11,\$11,0xffffffff4	24: beq \$t3, \$t3, start
<input type="checkbox"/>	0x00400030	0x216b0002	addi \$11,\$11,0x0000...	25: addi \$t3, \$t3, 2
<input type="checkbox"/>	0x00400034	0x08100000	j 0x00400000	27: j start

```
.text
start:
# ALU operations
li $t1, 1
li $t2, 2
add $t3, $t1, $t2
```



$$\text{start} = \text{PC} + 4 + \text{offset (in words)}$$

$$\rightarrow \text{offset} = -12_{10}$$

$$\begin{aligned}
 12_{10} &= && 0000 & 0000 & 0000 & 1100_2 \\
 -12_{10} &= && 1111 & 1111 & 1111 & 0011_2 \\
 &+ && 0000 & 0000 & 0000 & 0001_2 \\
 &= && 1111 & 1111 & 1111 & 0100_2 \\
 &= && \text{FFF4}_{16}
 \end{aligned}$$

beq Instruction encoding

0x0040002c | 0x116bfff4 | beq \$t1, \$t1, 0xffffffff | 24: | beq \$t3, \$t3, start

MIPS Reference Data

①



CORE INSTRUCTION SET

OPCODE
/ FUNCT
(Hex)

NAME, MNEMONIC	FOR-MAT	OPERATION (in Verilog)	OPCODE / FUNCT (Hex)
Add	add R	$R[rd] = R[rs] + R[rt]$	(1) 0 / 20 _{hex}
Add Immediate	addi I	$R[rt] = R[rs] + \text{SignExtImm}$	(1,2) 8 _{hex}
Add Imm. Unsigned	addiu I	$R[rt] = R[rs] + \text{SignExtImm}$	(2) 9 _{hex}
Add Unsigned	addu R	$R[rd] = R[rs] + R[rt]$	0 / 21 _{hex}
And	and R	$R[rd] = R[rs] \& R[rt]$	0 / 24 _{hex}
And Immediate	andi I	$R[rt] = R[rs] \& \text{ZeroExtImm}$	(3) c _{hex}
Branch On Equal	beq I	if($R[rs] == R[rt]$) PC=PC+4+BranchAddr	(4) 4 _{hex}
Branch On Not Equal	bne I	if($R[rs] != R[rt]$) PC=PC+4+BranchAddr	(4) 5 _{hex}

beq opcode = 4₁₆ = 000100₂
 \$t3 = \$11 = 01011₂
 offset = FFF4₁₆ = 1111 1111 1111 0100₂

encoding of beq \$t3, \$t3, start

= 000100 01011 01011 1111 1111 1111 0100₂
 = 0001 0001 0110 1011 1111 1111 1111 0100₂
 = 1 1 6 b f f f 4₁₆


- (1) May cause overflow exception
- (2) SignExtImm = { 16{immediate[15]}, immediate }
- (3) ZeroExtImm = { 16{1b'0}, immediate }
- (4) BranchAddr = { 14{immediate[15]}, immediate, 2'b0 }
- (5) JumpAddr = { PC+4[31:28], address, 2'b0 }
- (6) Operands considered unsigned numbers (vs. 2's comp.)
- (7) Atomic test&set pair; R[rt] = 1 if pair atomic, 0 if not atomic

BASIC INSTRUCTION FORMATS

R	opcode	rs	rt	rd	shamt	funct
	31	26 25	21 20	16 15	11 10	6 5
	0					
I	opcode	rs	rt	immediate		
	31	26 25	21 20	16 15		
	0					
J	opcode	address				
	31	26 25				
	0					

Implementing Jumps

Name	Fields						Comments
Field size	6 bits	5 bits	5 bits	5 bits	5 bits	6 bits	All MIPS instructions are 32 bits long
R-format	op	rs	rt	rd	shamt	funct	Arithmetic instruction format
I-format	op	rs	rt	address/immediate			Transfer, branch, imm. format
J-format	op	target address					Jump instruction format

 


- Jump uses **word** address (not byte address)
- Update (32 bit) PC with concatenation of
 - top 4 bits of (old PC + 4)
 - 26-bit jump address
 - 00
- Need extra control signal (for PC mux): decoded from opcode



0x00400034 | 0x08100000 | j | 0x00400000 | 27: | j | start

Implementing Jumps

INSTRUCTION MEMORY

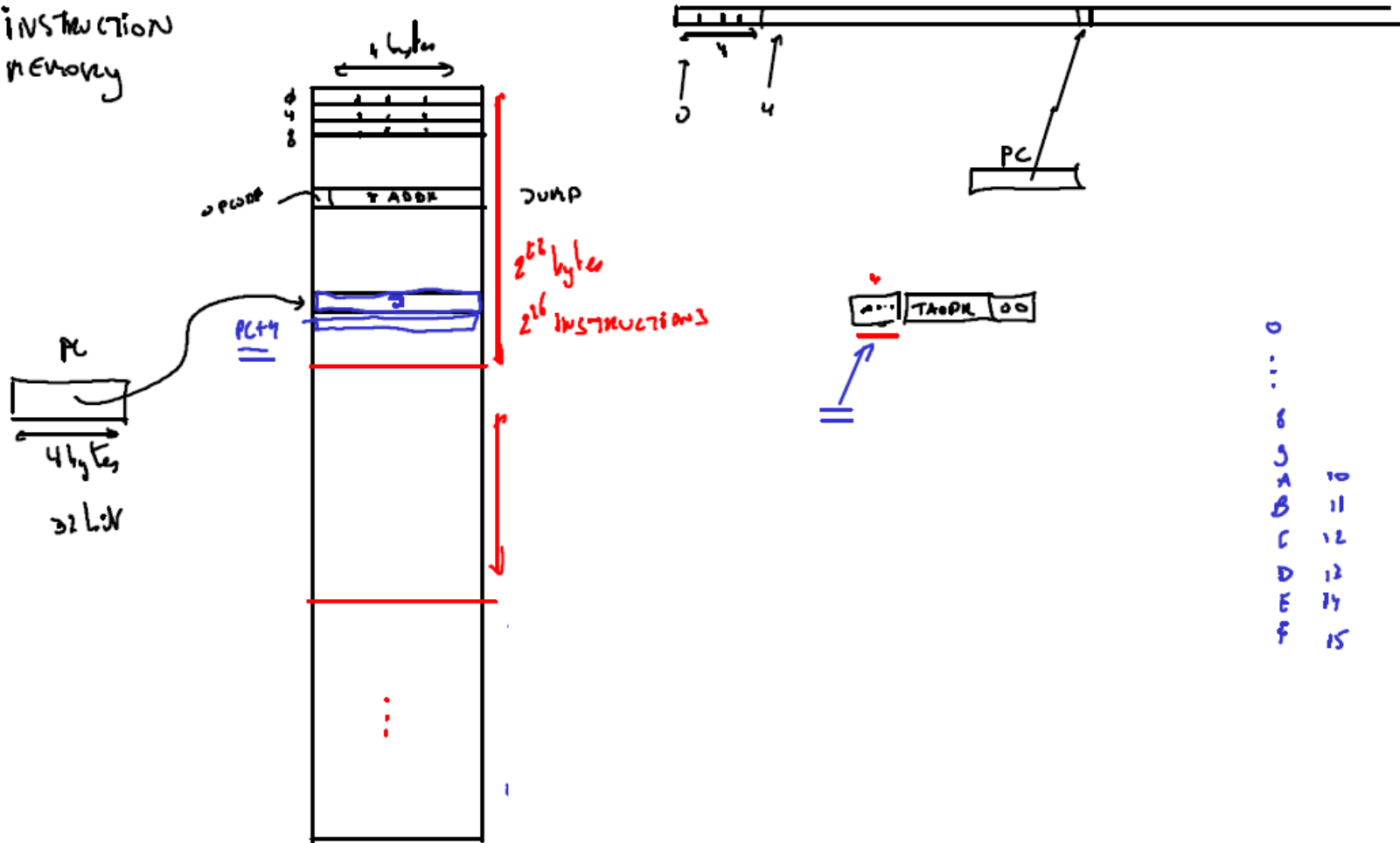

Implementing Jumps

  

jump Instruction encoding

0x00400034 0x08100000 j 0x00400000 27: j start

MIPS Reference Data

①



CORE INSTRUCTION SET

NAME, MNEMONIC	FOR-MAT	OPERATION (in Verilog)	OPCODE / FUNCT (Hex)
Add	add R	$R[rd] = R[rs] + R[rt]$	(1) 0 / 20 _{hex}
Add Immediate	addi I	$R[rt] = R[rs] + \text{SignExtImm}$	(1,2) 8 _{hex}
Add Imm. Unsigned	addiu I	$R[rt] = R[rs] + \text{SignExtImm}$	(2) 9 _{hex}
Add Unsigned	addu R	$R[rd] = R[rs] + R[rt]$	0 / 21 _{hex}
And	and R	$R[rd] = R[rs] \& R[rt]$	0 / 24 _{hex}
And Immediate	andi I	$R[rt] = R[rs] \& \text{ZeroExtImm}$	(3) c _{hex}
Branch On Equal	beq I	if($R[rs] == R[rt]$) $PC = PC + 4 + \text{BranchAddr}$	(4) 4 _{hex}
Branch On Not Equal	bne I	if($R[rs] != R[rt]$) $PC = PC + 4 + \text{BranchAddr}$	(4) 5 _{hex}
Jump	j J	$PC = \text{JumpAddr}$	(5) 2 _{hex}

j opcode = 2₁₆ = 000010₂

PC = 004000034₁₆

PC + 4 = 004000038₁₆

top 4 bits of (PC + 4)

= 0₁₆ = 0000₂

target address

= 00400000₁₆

= 0000 0000 0100 0000 0000 0000 0000 0000₂

26 bit address

encoding of j start

= 000010 0000 0100 0000 0000 0000 0000 00₂

= 0000 1000 0001 0000 0000 0000 0000 0000₂

= 0 8 1 0 0 0 0 0₁₆


- (1) May cause overflow exception
- (2) $\text{SignExtImm} = \{ 16\{\text{immediate}[15]\}, \text{immediate} \}$
- (3) $\text{ZeroExtImm} = \{ 16\{1b'0\}, \text{immediate} \}$
- (4) $\text{BranchAddr} = \{ 14\{\text{immediate}[15]\}, \text{immediate}, 2'b0 \}$
- (5) $\text{JumpAddr} = \{ PC+4[31:28], \text{address}, 2'b0 \}$
- (6) Operands considered unsigned numbers (vs. 2's comp.)
- (7) Atomic test&set pair; $R[rt] = 1$ if pair atomic, 0 if not atomic

start:

Bkpt	Address	Code	Basic	Source
<input type="checkbox"/>	0x00400000	0x24090001	addiu \$9,\$0,0x00000001	11: li \$t1, 1
<input type="checkbox"/>	0x00400004	0x240a0002	addiu \$10,\$0,0x0000...	12: li \$t2, 2
<input type="checkbox"/>	0x00400008	0x012a5820	add \$11,\$9,\$10	13: add \$t3, \$t1, \$t2
<input type="checkbox"/>	0x0040000c	0x3c011001	lui \$1,0x00001001	16: la \$t0, values
<input type="checkbox"/>	0x00400010	0x34280000	ori \$8,\$1,0x00000000	
<input type="checkbox"/>	0x00400014	0x8d090000	lw \$9,0x00000000(\$8)	17: lw \$t1, 0(\$t0)
<input type="checkbox"/>	0x00400018	0x8d0a0004	lw \$10,0x00000004(\$8)	18: lw \$t2, 4(\$t0)
<input type="checkbox"/>	0x0040001c	0x012a5820	add \$11,\$9,\$10	19: add \$t3, \$t1, \$t2
<input type="checkbox"/>	0x00400020	0x3c011001	lui \$1,0x00001001	20: la \$t0, result
<input type="checkbox"/>	0x00400024	0x34280008	ori \$8,\$1,0x00000008	
<input type="checkbox"/>	0x00400028	0xad0b0000	sw \$11,0x00000000(\$8)	21: sw \$t3, 0(\$t0)
<input type="checkbox"/>	0x0040002c	0x116bfff4	beq \$11,\$11,0xffffffff4	24: beq \$t3, \$t3, start
<input type="checkbox"/>	0x00400030	0x216b0002	addi \$11,\$11,0x0000...	25: addi \$t3, \$t3, 2
<input type="checkbox"/>	0x00400034	0x08100000	j 0x00400000	27: j start



Datapath With Jumps Added

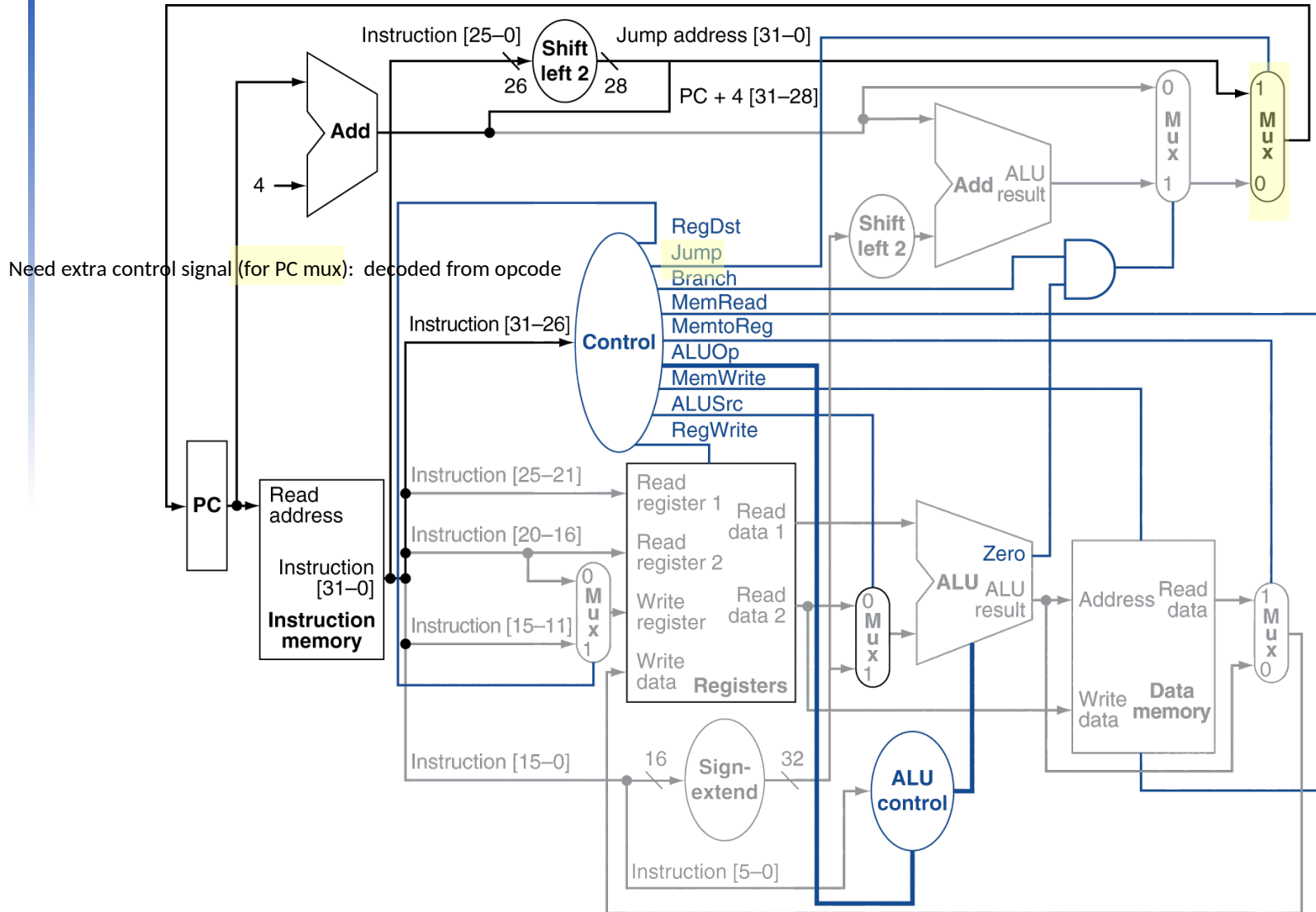

Performance Issues

- **Longest delay** determines **clock period**
 - **Critical** path: **load** instruction
 - Instruction memory → register file → ALU
→ data memory → register file
- Varying clock period for different instructions violates design principles:
 - **regularity**
 - **make the common case fast**
- Will improve performance by
Instruction-Level Parallelism (ILP) aka “pipelining”
(note that a constant clock period is needed for ILP)